

Ch. 30 – 27

27. (II) (a) In Fig. 30–28a, assume that the switch S has been in position A for sufficient time so that a steady current $I_0 = V_0/R$ flows through the resistor R . At time $t = 0$, the switch is quickly switched to position B and the current through R decays according to $I = I_0 e^{-t/\tau}$. Show that the maximum emf \mathcal{E}_{max} induced in the inductor during this time period equals the battery voltage V_0 . (b) In Fig. 30–28b, assume that the switch has been in position A for sufficient time so that a steady current $I_0 = V_0/R$ flows through the resistor R . At time $t = 0$, the switch is quickly switched to position B and the current decays through resistor R'

(which is much greater than R) according to $I = I_0 e^{-t/\tau'}$. Show that the maximum emf \mathcal{E}_{max} induced in the inductor during this time period is $(R'/R)V_0$. If $R' = 55R$ and $V_0 = 120 \text{ V}$, determine \mathcal{E}_{max} . [When a mechanical switch is opened, a high-resistance air gap is created, which is modeled as R' here. This Problem illustrates why high-voltage sparking can occur if a current-carrying inductor is suddenly cut off from its power source.]

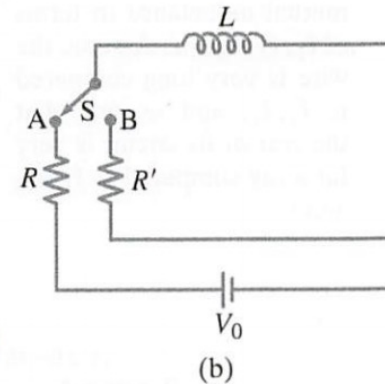
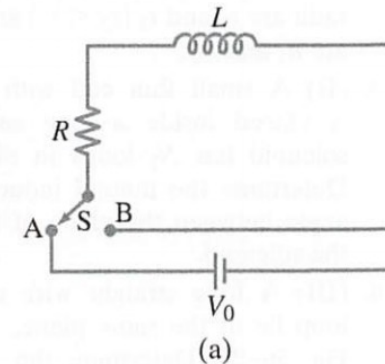


FIGURE 30–28
Problem 27.

Ch. 30 – 27

$$a) -L \frac{dI}{dt}$$


$$I = I_0 e^{-t/\tau} \\ = I_0 e^{-tR/L}$$

$$\mathcal{E} = -L \frac{dI}{dt} = -L \frac{d}{dt} (I_0 e^{-t/\tau})$$

$$= + \frac{L I_0 R}{L} e^{-t/\tau} = \underbrace{I_0 R}_{V_0} e^{-t/\tau}$$

$$\mathcal{E}_{\max} \text{ when } t=0$$

$$\mathcal{E}_{\max} = V_0$$

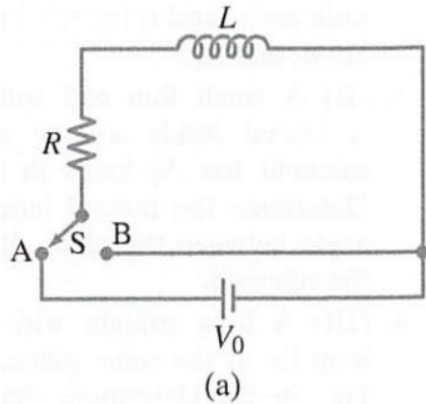

$$b) V_0 = I_0 R \Rightarrow I_0 = \frac{V_0}{R}$$

$$\mathcal{E} - IR' = 0$$

$$\mathcal{E} = IR' = R' I_0 e^{-t/\tau'} = \frac{R' V_0}{R} e^{-t/\tau'}$$

$$\mathcal{E}_{\max} = \frac{R' V_0}{R} = \frac{55R}{R} (120V) = 6.6 kV$$

