

a. 12 1Ω resistors in cube. Find effective resistance.



$$I_{initial} = 3A$$

$$V = IR$$

$$V_i - 1R - \frac{1}{2}R - 1R = V_f$$

$$V_i - 2\frac{1}{2}R = V_f$$

$$-2\frac{1}{2}R = V_f - V_i = \Delta V$$

$$\Delta V = I R_{eff} \Rightarrow -2.5R = 3 R_{eff}$$

$$R_{eff} = -\frac{2.5}{3}R$$

$$R = 1\Omega \quad \frac{5}{2} \cdot \frac{1}{3}$$

$$R_{eff} = -\frac{5}{6}\Omega = \frac{5}{6}\Omega$$

b. Now it is connected across C.



$$I_{in} = I_1 + I_2 + I_6$$

$$I_2 = I_5 + I_3$$

$$I_5 = I_{11} + I_{10}$$

$$I_{out} = I_1 + I_4 + I_8$$

$$I_3 + I_{12} = I_4$$

$$I_6 + I_{10} = I_7$$

$$I_{11} = I_{12} + I_9$$

$$I_7 + I_9 = I_8$$

8 nodes

$$I_{in} = I_1 + I_2 + I_6$$

$$I_2 = I_{11} + I_{10} + I_4 - I_{12} = I_{12} + I_9 + I_{10} + I_4 - I_{12} = I_9 + I_{10} + I_4$$

$$= I_9 + I_7 - I_6 + I_4 = I_9 - I_9 + I_6 - I_6 + I_4 = I_8 - I_7 + I_4$$

$$I_{in} = I_1 + I_8 - I_6 + I_4 + I_6 = I_1 + I_8 + I_4 = I_{out} \quad \checkmark$$

$$V = I_1 R$$

$$I_1 = I_2 + I_3 + I_4 = I_6 + I_7 + I_8 = I_2 + I_5 + I_{11} + I_9 + I_8$$

$$V = I_2 R + I_3 R + I_4 R$$

$$\Rightarrow I_1 = I_5 + 2I_3 + I_4 = I_5 + 3I_3 + I_{12} = I_2 - I_3 + 3I_3 + I_{12} = I_2 + 2I_3 + I_{12}$$

$$V = I_6 R + I_7 R + I_8 R$$

$$\Rightarrow I_1 = I_2 + I_2 - I_3 + I_{11} + I_9 + I_8 = 2I_2 - I_3 + I_{12} + 2I_9 + I_8$$


$$V = (I_2 + I_5 + I_{11} + I_9 + I_8) R$$

$$\Rightarrow I_2 + 2I_3 + I_{12} = 2I_2 - I_3 + I_{12} + 2I_9 + I_8$$


$$3I_3 = I_2 + 2I_9 + I_8$$

It doesn't ask to solve the whole thing so I am not going to solve that whole thing.

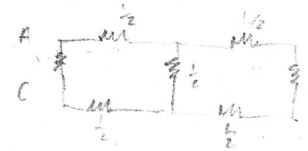We can't use the same geometry arguments as the current won't split evenly.



$$\frac{1}{2} + 2 = \frac{5}{2}$$

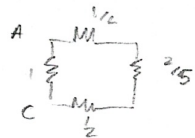

$$\frac{2}{3} + 1 = \frac{7}{3}$$



$$\frac{1}{R_{eff}} = 1 + \frac{9}{4} = \frac{13}{4}$$

$$R_{eff} = \frac{7}{12} \rightarrow \text{it decreases}$$